

Report of CS202 Final Project

Part 1. Introduction to Our CPU

(1) Cycle Design

We designed a multi-cycle CPU, whose implementation will be introduced in detail in **Part 2**.

(2) CPI

Since we have designed a multi-cycle CPU, our CPI varies from 2 to 4 according to different instructions.

(3) Reset Signal

Our reset signal is high-sensitive, which means our CPU will be reset to initial stage if the reset signal is high.

(4) Interfaces

Our CPU uses 23 switches, 17 LEDs, a 7-segment digital display tube as IO, and a UART transform interface.

K17 to **L21** is the 17 LEDs that used in outputting data.

Y9 is the reset switch, **w9** to **U6** is the 16 switches that used in inputting numbers, **w5** is the enable switch of 7-segment tube, **w6** is the enable switch of LED, **U5** is the switch used in switching test case 1 and test case 2, **T5**, **T4** and **R4** are the 3 switches used in switching mode in each test case.

w4 is the UART transform enable signal and **Y19** is the interface receiving UART data. Once the signal is high, all the sequential modules except the Instruction Memory will be reset. Then the Instruction Memory will be rewritten with the data that is transformed into FPGA through UART by **Y19**.

Part 2. Top Module Introduction

Our CPU's top module is actually a wrapper that wraps CPU and IO processors into one module (see **Part 4**.)

We call top module as **CPU wrap module** and the CPU top module (has all the sub-modules) as **CPU top module**.

In CPU wrap module, it get the raw input data from outside and send processed input data into CPU, also it will get the raw output data from CPU and send processed signals to LED and 7-segment tubes (see **Part 4**). This can reduce the coupling of our modules.

Figure 1. Connection of sub-modules

The diagram of inner connection of CPU top module is shown in Figure 1.

Part 3. Sub-module Introductions

(1) Clock divider

```
1 input clk_in;           // clock signal generated by oscillation in Y18
2 output clk_out;         // modified clock signal with lower frequency
```

Modify the oscillation in `Y18` into a signal with acceptable frequency.

(2) Instruction Fetcher

```
1 // inputs
2 // from ALU
3 input [31:0] Addr_result; // the calculated address
  from ALU
4 input Zero; // while Zero is 1, it means
  the ALU result is zero
5
6 input [31:0] read_data_1; // the address of
  instruction used by jr instruction
7 input Branch;
8 input nBranch;
9 input Jmp;
10 input Jal;
11 input Jr;
12 input clock;
13 input reset;
14 input Pause;
15 input IF_ena; // enable signal from FSA
  (see Part 5)
16
17 // uart inputs
18 input wire renew; // renew == 1 means CPU is
  rewriting instructions into memory
19 input wire [31:0] imem_write_data; // data transform into FPGA
  through UART
20 input wire [31:0] addr_pointer; // the address that a
  instruction from UART should be written to
21
22 // outputs
23 output [31:0] Instruction;
24 output [31:0] branch_base_addr; // (pc+4) to ALU which is
  used by branch type instruction
25 output [31:0] link_addr; // (pc+4) to decoder which
  is used by jal
```

Fetch instructions from instruction memory according to PC and update PC according to instruction. **It will update PC at positive edge and at every negative edge the instruction in memory will be read.**

(3) Decoder

```
1 // inputs
2 input [31:0] Instruction;
3 input [31:0] read_data;
4 input [31:0] ALU_result;
5 input [31:0] io_input; // input from outside (processed by
CPU wrap module)
6 input Jal; // 0 : data from alu, write to rt/rd
1 : data from pc + 4, write to $ra
7 input RegWrite; // write in register
8 input MemtoReg; // 1 : read data 0 : alu result
9 input RegDST; // 0 : rt 1 : rd
10 input clock, reset;
11 input [31:0] opcpus4; // from ifetch link_address
12 input ID_ena; // enable signal from FSA (see Part
5)
13 input WB_ena; // enable signal from FSA (see Part
5)
14
15 // outputs
16 output reg [31:0] read_data_1;
17 output reg [31:0] read_data_2;
18 output reg [31:0] imme_extend;
19 output reg [31:0] io_output; // output to the LED and 7-segment
tube
20 output reg Pause; // 1s stop signal
```

Sensitive to positive edge of clock signal. Decode the instruction, get data from registers and write data back to registers. **Also it will process the operation of I/O and pause** (see **Part 4**).

(4) Controller

```
1 // inputs
2 input [5:0] Opcode;
3 input [5:0] Function_opcode;
4
5 //outputs
6 output Jr;
7 output RegDST;
8 output ALUSrc;
9 output MemtoReg;
10 output Jmp;
11 output Jal;
12 output Branch;
13 output nBranch;
14 output RegWrite;
15 output MemWrite;
16 output I_format;
17 output Sftmd;
18 output [1:0] ALUOp;
19 output syscall; // whether the current instruction
is syscall (see Part 4)
```

Resolve the current instruction and send out control signals to the other modules.

(5) ALU

```
1 // inputs
2 // from decoder
3 input    [31:0] read_data_1;    // the source of Ainput
4 input    [31:0] read_data_2;    // one of the sources of Binput
5 input    [31:0] imme_extend;    // one of the sources of Binput
6 // from ifetch
7 input    [5:0] Function_opcode; // instructions[5:0]
8 input    [5:0] opcode;          // instruction[31:26]
9 input    [4:0] Shamt;           // instruction[10:6], the amount of
    shift bits
10 input    [31:0] PC_plus_4;     // pc + 4
11 // from controller
12 input    [1:0] ALUOp;          // { (R_format || I_format) ,
    (Branch || nBranch) }
13 input    ALUSrc;              // 1 means the 2nd operand is an
    immedite (except beq, bne)
14 input    I_format;            // 1 means I-Type instruction except
    beq, bne, LW, SW
15 input    Sftmd;               // 1 means this is a shift
    instruction
16 input    Jr;                  // 1 means this is a jr instr
17
18 // outputs
19 output    Zero;                // 1 means the ALU_result is zero, 0
    otherwise
20 output reg [31:0] ALU_Result;   // the ALU calculation result
21 output    [31:0] Addr_Result;   // the calculated instruction
    address
```

Calculate the result of mathematical operations and PC addresses.

(6) Data Memory

```
1 // inputs
2 input    clock;
3 input    [31:0] address;
4 input    [31:0] write_data;
5 input    Memwrite;             // control signal from controller
6 input    MEM_ena;              // enable signal from FSA (see Part
    5)
7 input    renew;                // uart mode signal
8 input    [31:0] uart_data;     // data read from uart
9 input    [31:0] uart_addr;     // uart data write address
10
11 // outputs
12 output    [31:0] read_data;
```

Read data according to address at every positive edge. Write data to specific address at positive edge while enable signal is high.

(7) UART Reader

```
1 // inputs
2 input          reset;
3 input          clock;
4 input          din;           // data transformed through UART,
    1 bit at one time
5
6 // outputs
7 output reg [31:0] imem_write_data; // data that should be written to
    memories
8 output reg [31:0] addr_pointer;    // the write address of a memory
```

Receives the data transformed by UART through `Y19`, one bit at each time at positive edge, and it will save it until it get 32 bits.

Send the write data and the address to the memory, the write data always corresponds to the address.

Once the UART reader receives 32 bit, it will refresh `imem_write_data` and `addr_pointer`.

(8) Tube Parser

```
1 // inputs
2 input          rst;
3 input          clk;
4 input [31:0]    input_num;      // raw output data from CPU (see
    Part 4)
5
6 // outputs
7 output reg [7:0] seg_en;        // 7-segment tube control signals
8 output reg [7:0] seg_out;      // 7-segment tube control signals
```

Parse the raw data in `io_output` into the signals that control the display of 7-segment tube (see **Part 4**).

At each positive edge, it will refresh `seg_en` and `seg_out` to display different numbers on the tube at different digits.

Part 4. `syscall` Instruction & I/O Design & Pause Design

Different from the IO design in PPT, we designed an architecture of IO imitating the `syscall` instruction in MIPS.

We added a new instruction `syscall`, which in machine code is `0xFFFFFFFF`.

Once the controller and decoder find that the current instruction is `syscall`, the controller will set `syscall` signal to high (this will be received by the FSA in the top module), and decoder will get the data in register `$v0`, and execute the input, output or pause process according to `$v0`. If `$v0 == 5` then input; if `$v0 == 1` then output; if `$v0 == 111` then pause for 1 second. The implementation is shown in Code 1.

```
1 // in decoder
2 if(Instruction == 32'hffff_ffff)
```

```

3  begin
4      if(Registers[2] == 32'd5)
5          Registers[2] <= io_input;
6      else if (Registers[2] == 32'd1)
7          io_output <= Registers[4];
8      else if (Registers[2] == 32'd111)
9          begin
10             if(counter == 32'h00af_79e0) // a counter used to count 11,500,000
cycles (1 second)
11                 begin
12                     Pause <= 1'b0;
13                     counter <= 32'h0000_0000;
14                 end
15             else
16                 begin
17                     Pause <= 1'b1;
18                     counter <= counter + 1'b1;
19                 end
20             end
21         end
22
23     // in controller
24     assign syscall = (Opcode == 6'b111111) ? 1'b1 : 1'b0;

```

Code 1. Syscall response

We will introduce input, output and pause in detail.

(1) Input

We added a new 32-bit port `io_input` in module decoder. The top wrap module receives the signals from the switches, process it into a 32-bit number and send it to `io_input` in decoder. The 32 bits respectively stand for:

- 1 `io_input[31]`: 1 represents the current case is testcase 2 and 0 represents testcase 1.
- 2 `io_input[30:28]`: The three input mode signals.
- 3 `io_input[27:16]`: No meaning, all set to 0.
- 4 `io_input[15:0]`: 16 input number signals.

Once the decoder finds `$v0 == 5`, it will assign `$v0` with the 32 bits in `io_input`, just the same as MIPS.

Then the input is read into `$v0` and we can process it through instructions.

(2) Output

We added a new 32-bit register-type port `io_output` as the output port in module decoder. Once the decoder finds `$v0 == 1`, it will assign `io_output` with the data in `$a0`, just like MIPS.

The `io_output` port will continuously send out signals to the top wrap module outside the CPU. There is one thing important that no matter the output device is 7-segment tube or LED, the data in `io_output` is the same.

```

1 // in module cpu_wrap, which is the upper module of CPU.
2 // For LED, we only need to output the lower 17 bits in io_output
3 assign led_out_sig = (led_output & ~reset) ? io_output[16:0] :
  17'b0_0000_0000_0000_0000;
4 assign seg_en = (tube_output & ~reset) ? seg_en_orig : 8'b1111_1111;
5 assign seg_out = (tube_output & ~reset) ? seg_out_orig : 8'b1111_1111;
6
7 Tube_Show ts( // This is a module that parses raw number into 7-segment
  signals
8             .rst(reset),
9             .clk(div_clk),
10            .input_num(io_output),
11            .seg_en(seg_en_orig),
12            .seg_out(seg_out_orig)
13            );

```

Code 2. Output signals

We know that to show a same number in 7-segment tube and LED, we need two groups of totally different signals. So the top module will parse the raw signal in `io_input` into signals that can be recognized by LED and 7-segment tube. The code is shown in Code 2, `led_output` and `tube_output` are the led enable signal and tube enable signal.

In instructions, we only need to assign `$a0` with the output number we want, set `$v0` to 1 and `syscall`, then the number in `$a0` will be shown in LED and 7-segment tube.

The advantage of this I/O design: reduced coupling. The input and output of CPU is standardized, and all the jobs that turns the signal into LED signal and 7-segment tube signals are done outside the CPU.

(3) Pause

When the decoder finds `$v0 == 111`, it will set signal `pause` to high and start a counter.

```

1 // in decoder
2 if(counter == 32'h00af_79e0) // 11,500,000
3 begin
4     Pause <= 1'b0;
5     counter <= 32'h0000_0000;
6 end
7 else
8 begin
9     Pause <= 1'b1;
10    counter <= counter + 1'b1;
11 end
12
13 // in instruction fetcher
14 if (IF_ena)
15 begin
16     if (Pause) // if paused, stop updating PC
17     begin
18     end
19     else if (Jal || Jmp)
20         PC <= {4'b0000, Instruction[25:0], 2'b00};
21     else
22         PC <= Next_PC;
23 end

```

Code 3. Pause design

Once the instruction fetcher finds that the `pause` signal is high, it will stop updating PC, keep PC pointing to the current instruction (i.e. `syscall`), so in the next stage `ID` decoder will keep decoding the `syscall` instruction and counting. The codes are shown in Code 3.

Until 11,500,000 cycles (1 second) have passed, the decoder will set pause to 0 and the instruction fetcher will restart to update PC again.

Part 5. Introduction to Multi-Cycle Design

To implement a multi-cycle CPU which can skip stages according to different instructions, we divided a instruction into 4 stages: `IF`, `ID`, `MEM` and `WB`.

Also, we added a finite state automata (FSA) into the CPU top module and the codes are shown in Code 4.

```
1  wire          IF_ena, ID_ena, MEM_ena, WB_ena;
2  assign IF_ena = (main_counter == 2'b00) ? 1'b1 : 1'b0;
3  assign ID_ena = (main_counter == 2'b01) ? 1'b1 : 1'b0;
4  assign MEM_ena = (main_counter == 2'b10) ? 1'b1 : 1'b0;
5  assign WB_ena = (main_counter == 2'b11) ? 1'b1 : 1'b0;
6
7  always @(posedge clock or posedge rst)
8  begin
9      if(rst)
10     begin
11         main_counter <= 2'b01;
12     end
13     else
14     begin
15         case (main_counter)
16             2'b00:
17                 main_counter <= 2'b01;
18             2'b01:
19                 begin
20                     if (syscall)
21                         // Since all the jobs using syscall are done in ID, we
22                         // can skip the stage MEM and WB
23                         main_counter <= 2'b00;
24                     else if (MemWrite)
25                         main_counter <= 2'b10;
26                     else if (RegWrite)
27                         main_counter <= 2'b11;
28                     else
29                         main_counter <= 2'b00;
30                 end
31             2'b10:
32                 begin
33                     if (RegWrite)
34                         main_counter <= 2'b11;
35                     else
36                         main_counter <= 2'b00;
37                 end
38             2'b11:
39                 begin
40                     if (MemWrite)
41                         main_counter <= 2'b10;
42                     else
43                         main_counter <= 2'b00;
44                 end
45         endcase
46     end
47 end
```



```

37         2'b11:
38             main_counter <= 2'b00;
39         endcase
40     end
41 end

```

Code 4. FSA design

The FSA receives the control signals such as `reg_write`, `mem_write`, `syscall` from the controller, and send out enable signals to the sub-modules. Once a positive edge of the clock comes, a module can execute only when it has the enable signal from the controller and the FSA at the same time. The state diagram is shown in Figure 1.

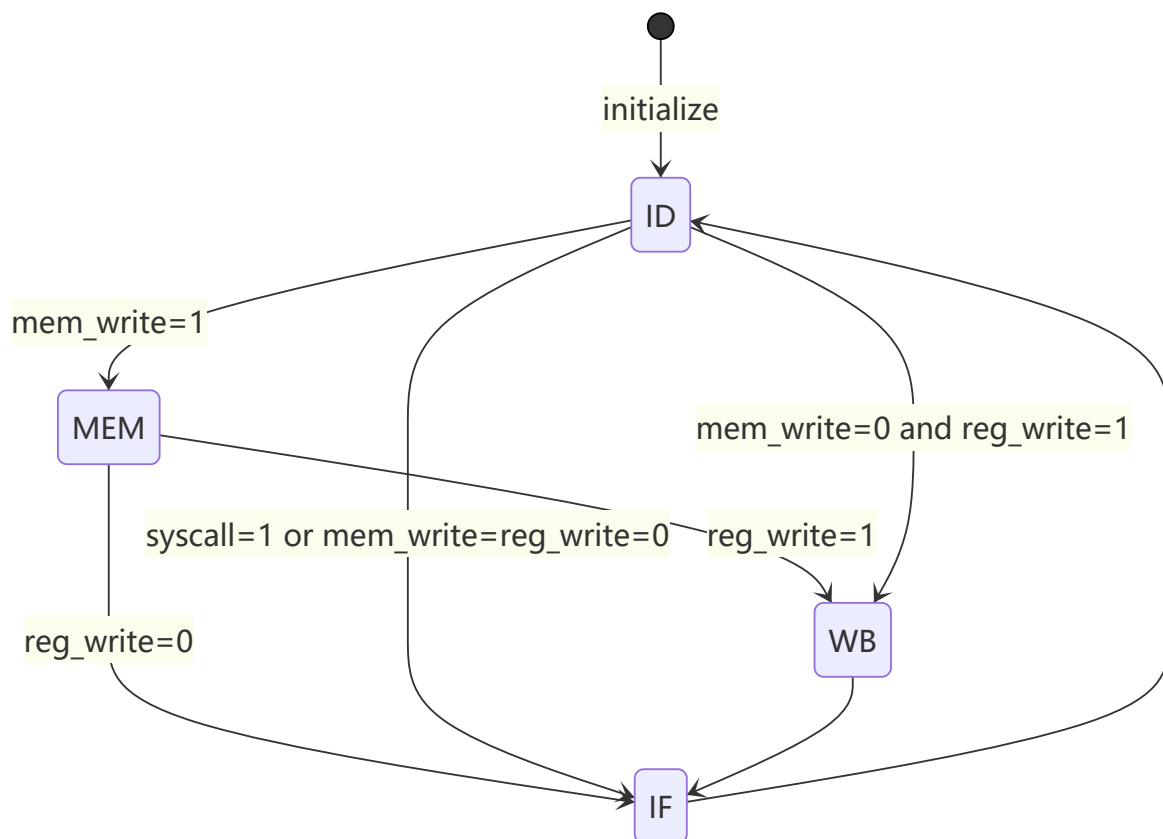


Figure 1. State Diagram of FSA

The initial state is ID, because in `IF` stage we designed to update PC, but at the initial state PC already points at the first instruction so we should not update it.

Using this design, we implemented a multi-cycle CPU that can skip stages according to different instructions.

Part 6. Problems & Solutions

Problem 1: In our design, reading from registers is a sequential process, and this is because we didn't realize that this can be done without clock signal. As a result, to avoid data disorder we must use more than 1 cycle to finish a instruction.

Solution 1: We designed a multi-cycle CPU and divided a instruction into 4 stages. Though in our perspective this is design is as good as single-cycle, we paid a lot of time to modify the CPU into a multi-cycle one, such as adding FSA, adding new control signals. From this experience we have learnt that it's important to have a compact analysis before coding.

Problem 2: Sometimes the simulation result is not the same as what FPGA shows in the real case.

Solution 2: We did troubleshooting by testing each sub-module separately on FPGA and finally find the module having problem. We will usually reduce the coupling among modules to solve problems and this usually works. This taught us that is important to reduce the coupling among modules: this can not only make it easier to find the problem but can also lower the distortion rate.